

Because the current goes through Q_1 , $V_{E6} \rightarrow V_{B6}$ will drop 0.7V to satisfy saturation. $V_{E1} \rightarrow V_{B1}$ will drop 0.2V

Given by V_{DD} 5V,

$$V_{B6} = V_{DD} - V_{BE} = 5V - 0.7V = 4.3V,$$

$$V_{C6} = V_{DD} - V_{CE} = 5V - 0.2V = 4.8V$$

For Q_1 ,

$$V_{B1} = V_{E1} - V_{BE} = V_{C6} - V_{BE} = 4.8 - 0.7 = 4.1V$$

$$V_{C1} = V_{E1} - V_{CE} = V_{C6} - V_{CE} = 4.8 - 0.2 = 4.6V$$

For Q_6

$$I_{C6} = \beta I_{B6},$$

For point C_1 there has 8 parallel LED for one 7-segment, $I_{C1}' = 8 I_C$

For point C_6 there has 5 parallel PNP, $I_{C6} = 5 I_{E1}$

$$I_{C1}' = \frac{\beta}{1+\beta} I_{E1} = \frac{\beta I_{C6}}{(1+\beta)5} = \frac{\beta}{5(1+\beta)} I_{B6} \Rightarrow I_{C1}' \approx \frac{\beta}{5} I_{B6} \Rightarrow I_{B6} \approx \frac{5}{\beta} I_{C1}'$$

$$I_{B1} = \frac{I_{E1}}{1+\beta} = \frac{1}{5(1+\beta)} I_{C6} = \frac{\beta}{5(1+\beta)} I_{B6} \Rightarrow I_{B1} \approx \frac{I_{B6}}{5}$$

Assuming the max current which goes through LED is 10mA, $\beta=100$, the voltage drop of L1 is 2V


$$R_7 = \frac{V_{C1} - 2}{I_{C1min}} = \frac{4.6 - 2}{10mA} = 260 \Omega.$$

So choose 270 Ω in the circuit.
for $R_7 - R_{14}$.

$$R_1 = \frac{V_{B1} - 0}{I_{B1}} = \frac{V_{B1} \beta}{I_{C1}} = \frac{4.3 \times 100V}{8 \times 10mA} = 5.375k\Omega, \text{ So choose } 4.7k\Omega \text{ for } R_1 \sim R_5$$

$$R_5 = \frac{V_{B6} - 0}{I_{B6}} = \frac{V_{B6} \beta}{I_{C1}'} = \frac{4.3 \times 100V}{8 \times 10mA} = 5.375k\Omega \text{ choose } 4.7k\Omega \text{ in the circuit.}$$

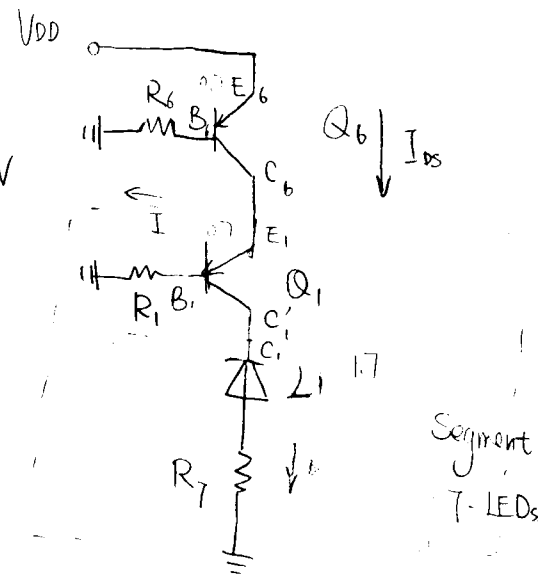According to ATmega128 Datasheet, each I/O port can sink 20mA at $V_{CC} = 5V$. It's more than the current that I design. So, using those resistors for LEDs/ buttons is safe.



Actually measurements

For LED 1 (7-segment a).

$$I_a = 23.8 \text{ mA}$$

However, the LED a becomes lighter when I test than it enlights in normal. I think the current of LED is influenced by the multimeter, which has power to increase the measuring current I_a . It differs from the value I calculate.

When the value of digit display is more than 1023, it will subtract 1023 and display the remainder.